 



CSE 308: Digital System Design

- (a) State whether the following FSM is a Moore/Mealy FSM. Explain why?
- (b) Convert the FSM to its other form.
- (c) Implement the FSM in (a) in Verilog.



Solution:

 - (a) The given FSM is a Moore FSM because the output depends on present state only.
- (b) Moore \rightarrow Mealy.



(c)

```
module reduce (clk, reset, in, out);
    input clk, reset, in;
    output out;
    parameter zero = 0, one1 = 1, twols = 2; // states
    reg out;
    reg [1:0] state; // state register
    reg [1:0] next_state; // always block needs reg

    // Implement the state register
    always @(posedge clk)
        if (reset) state = zero; //can put in next state logic
        else state = next_state;

    always @(in or state) // combinational logic
    case (state)
        zero: begin // last input was a zero
            out = 0;
            if (in) next_state = one1;
            else next_state = zero;
        end
        one1: begin // we've seen one 1
            out = 0;
            if (in) next_state = twols;
            else next_state = zero;
        end
        twols: begin // we've seen at least 2 ones
            out = 1;
            if (in) next_state = twols;
            else next_state = zero;
        end
        default: begin // in case we reach a bad state
            next_state = zero;
            out = 0;
        end
    endcase
endmodule
```

must include all signals
that are input to state
and output equations

