

Digital Logic Design

Chapter 5: Sequential Circuits Design

Sequential Logic

Logic That Remembers

Sequential Logic

- Memory added to Combinational Logic
- Memory elements: Output is held in One of Two Stable States
 - Latches
 - Flip Flops
- Identified by the presence of Feedback
- Output depends on Inputs & State of the Circuit

Digital Logic Design Fall 2005 Lecture 14

Sequential Logic Circuits

- Classification
 - Synchronous: External timing signal determines output updates
 - Asynchronous: Outputs are updated following changes in state or inputs after propagation delays
- Structural Classification:
 - Moore: Output only derived from Flip Flops
 - Mealy: Output is combinational function of Flip Flops and inputs

Digital Logic Design Fall 2005 Lecture 14

Hazards and Sequential Logic


- In synchronous sequential circuits, most of the glitches that may occur do not cause problems because they occur in the part of the clock cycle where they do not affect the flip-flops.
- However, in asynchronous sequential circuits changes occurring at any time can affect the signals on the feedback loops and cause the circuit to enter in an incorrect state.

Digital Logic Design Fall 2005 Lecture 14

Latches

- Binary Storage Elements
 - Asynchronous in nature: No Clock
 - Types include SR and D
 - NOR and NAND implementations possible


| Set | Reset | Q | Qbar | |
|-----|-------|---|------|--------------------------|
| 1 | 0 | 1 | 0 | Latch in Set State |
| 0 | 0 | 1 | 0 | |
| 0 | 1 | 0 | 1 | Reset State of the Latch |
| 0 | 0 | 0 | 1 | |
| 1 | 1 | 0 | 0 | Next State is Undefined |

 

Digital Logic Design Fall 2005 Lecture 14

NAND Implementation of Latch

| Set | Reset | Q | Qbar | |
|-----|-------|---|------|--------------------------|
| 0 | 1 | 1 | 0 | Latch in Set State |
| 1 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 1 | Reset State of the Latch |
| 1 | 1 | 0 | 1 | |
| 0 | 0 | 1 | 1 | Next State is Undefined |

 


Digital Logic Design Fall 2005 Lecture 14

The Clocked Latch

- A control input (called Clock) is added
 - Output changes only when this input is HIGH
 - Allows more control over the time when state changes are required

| Clock | Set | Reset | Q | Qbar | |
|-------|-----|-------|---|------|--------------------------------|
| 0 | X | X | 1 | 0 | No change: Previous state held |
| 1 | 0 | 0 | 1 | 0 | |
| 1 | 0 | 1 | 0 | 1 | Reset State |
| 1 | 1 | 0 | 1 | 0 | Set State |
| 1 | 1 | 1 | 1 | 1 | Undefined |

 


Digital Logic Design Fall 2005 Lecture 14

The D Latch


- Avoids ambiguous inputs
- Used as Data (*D*) storage device enabled by the clock
- Also called a **Transparent Latch**

| Clock | D | Q | |
|-------|---|---|--------------------------------|
| 0 | X | 0 | No change: Previous state held |
| 1 | 0 | 0 | Reset State |
| 1 | 1 | 1 | Set State |

 

Digital Logic Design Fall 2005 Lecture 14

D Latch Symbol

 


| En | D | Q | Qbar |
|----|---|----|------|
| 0 | X | NC | NC |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

NC: No Change

Digital Logic Design Fall 2005 Lecture 14


Latch is Transparent

 - D Latch is called “transparent” or “level sensitive”
- Output follows input instantaneously




Digital Logic Design Fall 2005 Lecture 14

Transparency Property

 

Digital Logic Design Fall 2005 Lecture 14


Problem of Transparency

 

- A momentary input change tunnels through the latch and the entire circuitry
- What problem this can cause?


Digital Logic Design Fall 2005 Lecture 14

Problem of Transparency

 

Digital Logic Design Fall 2005 Lecture 14

Eliminating Transparency

 

- Separating the input and output, so they are independently controlled
- Only open one gate at a time to avoid tunneling


Digital Logic Design Fall 2005 Lecture 14

The Flip Flop

- Two ways to design F/F
 - Construction Methods
 - Master Slave
 - Edge-Triggered
- Master Slave F/F
 - Two Cascaded Latches and an Inverter
 - First Latch is enabled during High time of the Clock
 - Second Latch is enabled during Low time of Clock
- Edge Triggered Latch
 - Outputs can change only at the Transition of Clock
 - Hi-to-Low (falling) and Low-to-High (rising) Edge
- Designed for Synchronous Logic
 - Time Window for Data to Pass to the Output is Extremely Short

Digital Logic Design Fall 2005 Lecture 14


Flip-Flop (F/F)

 

Digital Logic Design Fall 2005 Lecture 14


The Master-Slave SR Flip Flop

 - Two Cascaded Latches and an Inverter
 - First Latch is enabled during High time of the Clock
 - Second Latch is enabled during Low time of Clock




Digital Logic Design Fall 2005 Lecture 14


Behavior of Master-Slave FF

 


Behavior of Master-Slave FF

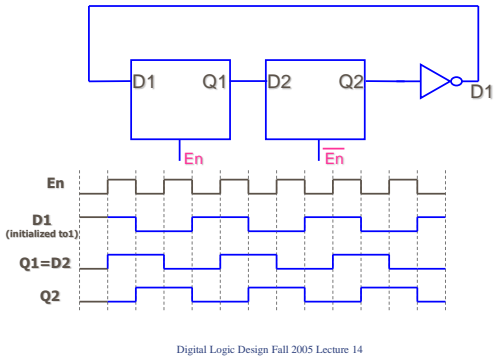

Behavior of Master-Slave FF

 

Behavior of Master-Slave FF

 

The JK Flip Flop


- SR Flip Flop or Latch has *One Prohibited* input State
- JK overcomes the SR limitation of both inputs being asserted simultaneously
- The Behavior is described by the following Table
 - Both J and K being TRUE cause a TOGGLE of the State

| J | K | Next State |
|---|---|------------|
| 0 | 0 | Q |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q' |

Digital Logic Design Fall 2005 Lecture 14


The JK Flip Flop

 - Two AND gates added to the SR FF
 - The current state of the FF allows the RIGHT input to pass through




D-type ↓ Edge Triggered Flip Flop

- Cascade of a D and an SR Latch

 


Digital Logic Design Fall 2005 Lecture 14

Flip Flops Symbols

 

Positive Edge Triggered
D Flip Flop

 

Negative Edge Triggered
D Flip Flop

Digital Logic Design Fall 2005 Lecture 14

Important FF Parameters

- Setup Time: Minimum time that the input e.g. D must be present and stable **before** the clock edge
- Hold Time: Minimum time that the input e.g. D must be held stable **after** the clock edge
 - A violation of Setup or Hold Time will result in unpredictable outputs
- Propagation Delay or Clock to Q delay:
 - The time after the clock edge to the output being stable in the new state

Digital Logic Design Fall 2005 Lecture 14

The Characteristic Table

- Defines the Logical Properties of the Flip Flop
- Similar to the Truth Table for Combinational Circuits

| S | R | Next State $Q(t+1)$ |
|---|---|---------------------|
| 0 | 0 | Hold |
| 0 | 1 | Reset |
| 1 | 0 | Set |
| 1 | 1 | Undefined |

| J | K | Next State $Q(t+1)$ |
|---|---|---------------------|
| 0 | 0 | Hold |
| 0 | 1 | Reset |
| 1 | 0 | Set |
| 1 | 1 | Toggle |

| D | Next State $Q(t+1)$ |
|---|---------------------|
| 0 | Reset |
| 1 | Set |

| T | Next State $Q(t+1)$ |
|---|---------------------|
| 0 | Hold |
| 1 | Toggle |

Digital Logic Design Fall 2005 Lecture 14

Sequential Circuit Analysis




- Label All Flip Flop Outputs (arbitrarily)
- Write Equations describing combinational logic leading to all Flip Flop Inputs
- Determine the FF Outputs from Characteristic Table
- Complete the **State Table**
 - Present State: Inputs: Next State: Outputs
- Circuit with m FF and n inputs need 2^{m+n} entries in the **State Table**

Digital Logic Design Fall 2005 Lecture 14


State Table

- The table shows the present states, inputs, next states and outputs
- One Dimensional (present state and inputs combined) Moore Model
- Two Dimensional (present state left column and inputs tabulated across the top) Mealy Model

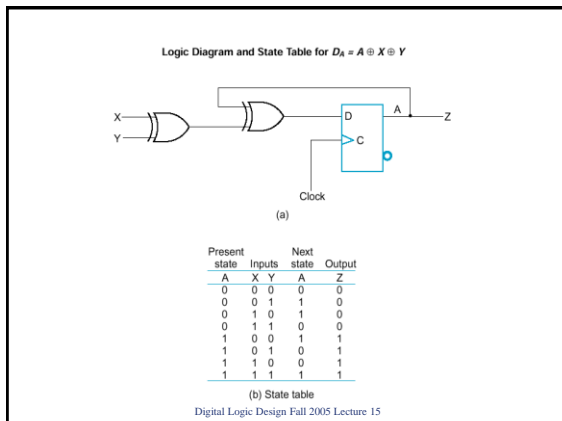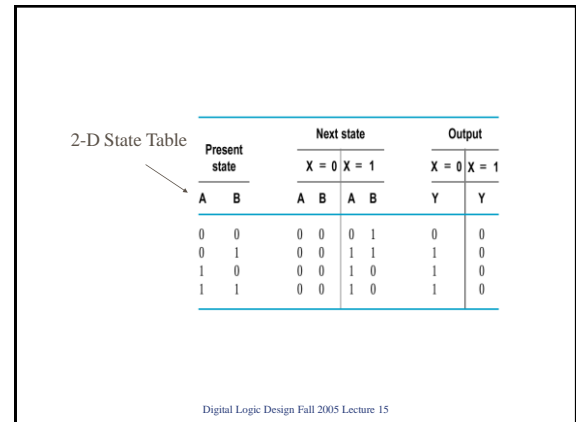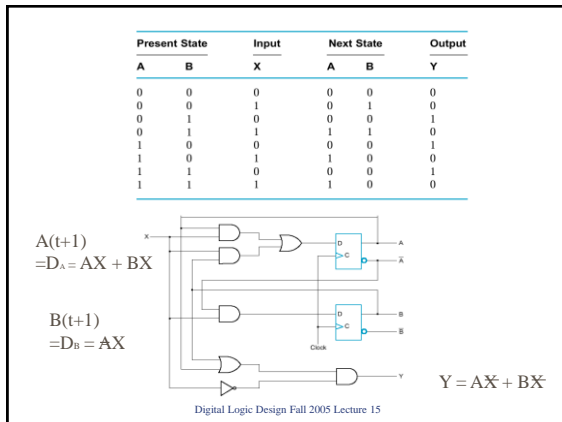Digital Logic Design Fall 2005 Lecture 15



Sequential Circuit Analysis: Example

 

Sequential Circuit Analysis: Example

- Find the Flip Flop Input Equations

$$J_A = BX + \overline{B}\overline{Y} \quad K_A = \overline{B}XY$$

$$J_B = \overline{A}X \quad K_B = A + X\overline{Y}$$

- Find the Output Equations

$$Z = AXY + B\overline{X}\overline{Y}$$


- Determine the Next State of the Flip Flops from Characteristic Tables
- Fill the State Table
- Draw the State Diagram

Digital Logic Design Fall 2005 Lecture 15

State and State Diagram


- A **state** represents the machine snapshot at a given clock period
 - A clock is typically used to **synchronize** the state transition
 - A graph consists of a set of
 - Circles:
 - Each represents a **state**
 - Use double circle to represent the **initial state**
 - Directed arc: each represents a state transition
 - Inputs/outputs
 - Mealy machine:
 - Label **input/output** along each arc
 - Moore machine:
 - Label **input** along each arc
 - Label **output** inside the circle (i.e. state)
- Digital Logic Design Fall 2005 Lecture 15

Mealy and Moore Machines

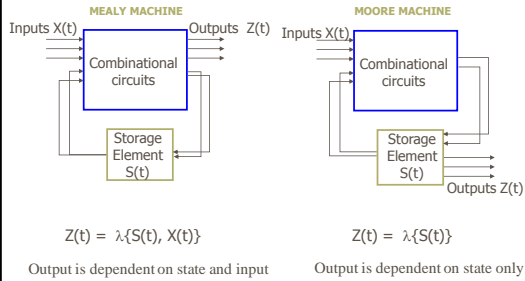

Digital Logic Design Fall 2005 Lecture 15

State Diagrams

 

Example:

State: $S(t) \in \{S_k, S_j\}$


Inputs: $X(t) \in \{a, b\}$

Outputs: $Z(t) \in \{p, q\}$

Initial state: $S(0) = S_k$


Digital Logic Design Fall 2005 Lecture 15

State Diagram Examples (Mealy)

 

Digital Logic Design Fall 2005 Lecture 15

State Diagram Examples (Moore)

 

Digital Logic Design Fall 2005 Lecture 15

Design Example: Sequence Recognizer

- A sequential circuit that recognizes the occurrence of a particular bit sequence
- Input: $X(t) \in \{0, 1\}$
- Output: $Z(t) \in \{0, 1\}$

$$Z(t) = \begin{cases} 1, & \text{if } X(t-3, t) = 1101 \\ 0, & \text{Otherwise} \end{cases}$$

Digital Logic Design Fall 2005 Lecture 16


Sequence Recognizer

$$Z(t) = \begin{cases} 1, & \text{if } X(t-3, t) = 1101 \\ 0, & \text{Otherwise} \end{cases}$$

| Time | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 |
|--------|---|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|
| $X(t)$ | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| $Z(t)$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |

Digital Logic Design Fall 2005 Lecture 16

State Diagram & State Table

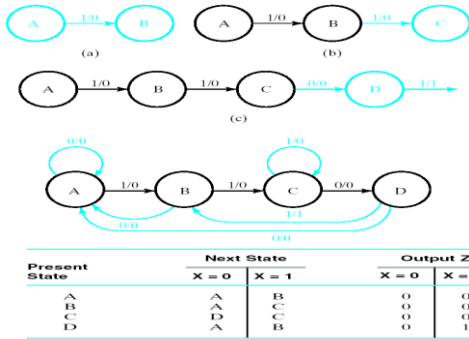


Digital Logic Design Fall 2005 Lecture 16


Sequence Recognizer

$$Z(t) = \begin{cases} 1, & \text{if } X(t-3, t) = 1101 \\ 0, & \text{Otherwise} \end{cases}$$

| | | | | | | | | | | | | | | | | | |
|------|---|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|
| Time | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 |
| X(t) | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| Z(t) | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | |

 A Mealy Machine
Digital Logic Design Fall 2005 Lecture 16

State Table

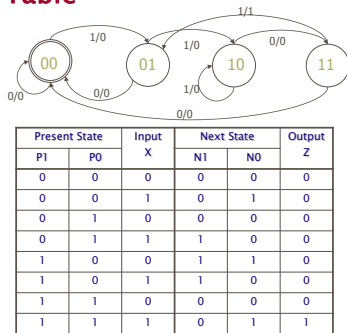


Digital Logic Design Fall 2005 Lecture 16

Logic Circuits Design Steps

- Obtain state diagram or state table as requirement
- Assign binary codes to states
 - Each external output
 - Each state encoded bit
- Simplify the Boolean functions
- Draw a D F/F (or register) for each state encoded bit
 - External outputs
 - Each inputs of state encoded bits
 - Input of state encoded bits = the next state
 - Output of state encoded bits = the current state


Digital Logic Design Fall 2005 Lecture 17

Logic Circuits Design

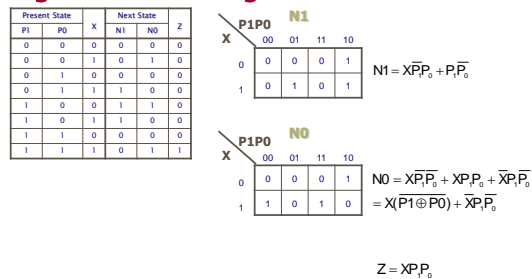

Digital Logic Design Fall 2005 Lecture 17

Logic Circuits Design

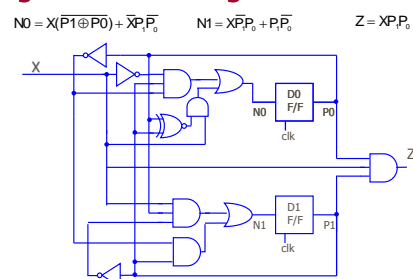

Digital Logic Design Fall 2005 Lecture 17

Vending Machine State Machine

- Dispense a Coke when depositing 15 ¢

Inputs


- 5 = a nickel
- 10 = a dime
- BC = bad coin (including quarters in this example)

Outputs

- R = reject
- C = coke
- N = no coke


Digital Logic Design Fall 2005 Lecture 18

State Diagram

 

Digital Logic Design Fall 2005 Lecture 18

State Table

 

| Present State (0¢, 5¢, 10¢) | | Input (5¢, 10¢, BC) | | Next State (0¢, 5¢, 10¢) | | Output (C, N, R) | |
|--------------------------------|----|------------------------|----|-----------------------------|----|---------------------|----|
| P1 | P0 | X1 | X0 | N1 | N0 | C1 | C0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |

Digital Logic Design Fall 2005 Lecture 18

Logic Circuits Design

| Present State | | Input | | Next State | | Output | |
|---------------|----|-------|----|------------|----|--------|----|
| P1 | P0 | X1 | X0 | N1 | N0 | C1 | C0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | X | X | X | X | X | X |

| X1X0 | | N1 | |
|------|-------------|-------------|--|
| P1P0 | 00 01 11 10 | 00 01 11 10 | |
| 00 | 0 1 X 0 | | |
| 01 | 1 0 X 0 | | |
| 11 | X X X X | | |
| 10 | 0 0 X 1 | | |

$$N1 = P0X1X0 + \overline{P1}P0X0 + P1X1$$

| X1X0 | | N0 | |
|------|-------------|-------------|--|
| P1P0 | 00 01 11 10 | 00 01 11 10 | |
| 00 | 1 0 X 0 | | |
| 01 | 0 0 X 1 | | |
| 11 | X X X X | | |
| 10 | 0 1 X 0 | | |

$$N0 = P1P0X1X0 + P1X0 + P0X1$$

Digital Logic Design Fall 2005 Lecture 18

Logic Circuits Design

| Present State | | Input | | Next State | | Output | |
|---------------|----|-------|----|------------|----|--------|----|
| P1 | P0 | X1 | X0 | N1 | N0 | C1 | C0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | X | X | X | X | X | X |

| X1X0 | | C1 | |
|------|-------------|-------------|--|
| P1P0 | 00 01 11 10 | 00 01 11 10 | |
| 00 | 0 0 X 1 | | |
| 01 | 0 0 X 1 | | |
| 11 | X X X X | | |
| 10 | 0 0 X 1 | | |

$$C1 = X1$$

| X1X0 | | C0 | |
|------|-------------|-------------|--|
| P1P0 | 00 01 11 10 | 00 01 11 10 | |
| 00 | 0 0 X 0 | | |
| 01 | 0 1 X 0 | | |
| 11 | X X X X | | |
| 10 | 1 1 X 0 | | |

$$C0 = P1X1 + P0X0$$

Digital Logic Design Fall 2005 Lecture 18


Logic Circuits for Vending Machine

$$N1 = P0X1X0 + \overline{P1}P0X0 + P1X1$$

$$N0 = P1P0X1X0 + P1X0 + P0X1$$

$$C1 = X1$$

$$C0 = P1X1 + P0X0$$

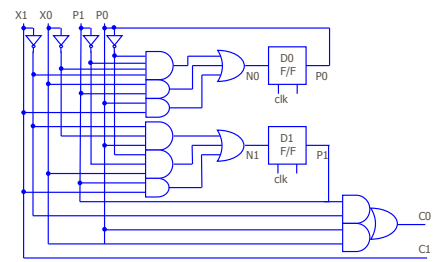

Digital Logic Design Fall 2005 Lecture 18