 


- (a) Design a Moore FSM that outputs a 1 when three consecutive 1's have been received as input and 0 otherwise.
- (b) Implement the FSM in (a) in Verilog.

Solution:

(a)



(b)

```

module seq3_detect_moore(x,clk, y);
// Moore machine for a three-1s sequence detection
input x, clk;
output y;
reg [1:0] state;
parameter S0=2'b00, S1=2'b01, S2=2'b10,
S3=2'b11;
// Define the sequential block
always @(posedge clk)
    case (state)
        S0: if (x) state <= S1;
            else state <= S0;
        S1: if (x) state <= S2;
            else state <= S0;
        S2: if (x) state <= S3;
            else state <= S0;
        S3: if (x) state <= S3;
            else state <= S0;
    endcase
// Define output during S3
    assign y = (state == S3);
endmodule
  
```

