

## Digital Logic Design

### Chapter 2 Boolean Algebra and Logic Gates


## Combinational Logic Circuits

- Logic Gates: Control the flow of information
- Represent Logical Operations (Functions)
  - Inputs are like arguments to a function
  - Outputs are like result of the function
  - Fundamental Set
    - AND
    - OR
    - NOT
    - Transmission Gate
- Truth Tables...


Digital Logic Design - Chapter 2

2

## Digital Logic Gates

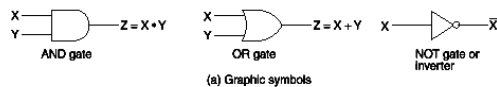

(a) Graphic symbols

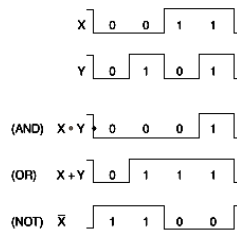


(b) Timing diagram


Digital Logic Design - Chapter 2

3

## Gates with more than Two Inputs

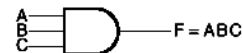

(a) Three-input AND gate

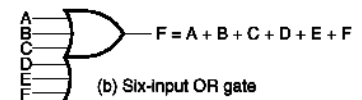


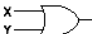


(b) Six-input OR gate

Digital Logic Design - Chapter 2

4

## Digital Logic Gates





Graphics Symbols

Name	Distinctive shape	Algebraic equation	Truth table															
AND		$F = XY$	<table><tr><td>X</td><td>Y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	X	Y	F	0	0	0	0	1	0	1	0	0	1	1	1
X	Y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = X + Y$	<table><tr><td>X</td><td>Y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	1
X	Y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT (inverter)		$F = \overline{X}$	<table><tr><td>X</td><td>F</td></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	X	F	0	1	1	0									
X	F																	
0	1																	
1	0																	
Buffer		$F = X$	<table><tr><td>X</td><td>F</td></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	X	F	0	0	1	1									
X	F																	
0	0																	
1	1																	

Digital Logic Design - Chapter 2

5

Graphics Symbols

Name	Distinctive shapes	Rectangular shapes	Algebraic equation	Truth table															
NAND			$F = \overline{X \cdot Y}$	<table><tr><td>X</td><td>Y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	X	Y	F	0	0	1	0	1	1	1	0	1	1	1	0
X	Y	F																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	
NOR			$F = \overline{X + Y}$	<table><tr><td>X</td><td>Y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	0
X	Y	F																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	0																	
Exclusive-OR (XOR)			$F = X\overline{Y} + \overline{X}Y$ $= X \oplus Y$	<table><tr><td>X</td><td>Y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	0
X	Y	F																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	
Exclusive-NOR (XNOR)			$F = XY + \overline{X}\overline{Y}$ $= \overline{X \oplus Y}$	<table><tr><td>X</td><td>Y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	1
X	Y	F																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	1																	

Digital Logic Design - Chapter 2

6

## Boolean Algebra

- Algebra is a complete set of rules defined on some variables.
- Variables can be Real or Logical: This subject deals with Logical Variables
- A Logical Variable can take one of two values
- A Logical Function is represented by
  - Truth Tables
  - Boolean Expressions

Digital Logic Design - Chapter 2

7

## What is Boolean Algebra

- An algebra dealing with
  - Binary variables by alphabetical letters
  - Logic operations: OR, AND, XOR, etc
- Consider the following Boolean equation

$$F(X, Y, Z) = \overline{X} \cdot \overline{Y} + \overline{Y} \cdot \overline{Z} + Z$$

- A Boolean function can be represented by a truth table which list all combinations of 1's and 0's for each binary value

Digital Logic Design - Chapter 2

8

## Fundamental Operators

### ■ NOT

- Unary operator
- Complements a Boolean variable represented as  $A'$ ,  $\sim A$ , or  $\bar{A}$

### ■ OR

- Binary operator
- A ORed with B is represented as  $A + B$

### ■ AND

- Binary operator
- A ANDed with B is represented as  $AB$  or  $A \cdot B$
- Can perform logical multiplication

Digital Logic Design - Chapter 2

9

## Binary Boolean Operations

- All possible outcomes of a 2-input Boolean function

A	B	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>	F <sub>5</sub>	F <sub>6</sub>	F <sub>7</sub>	F <sub>8</sub>	F <sub>9</sub>	F <sub>10</sub>	F <sub>11</sub>	F <sub>12</sub>	F <sub>13</sub>	F <sub>14</sub>	F <sub>15</sub>
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

NULL (F<sub>0</sub>),  $A \cdot B$  (F<sub>1</sub>),  $A$  (F<sub>4</sub>),  $A \oplus B$  (F<sub>5</sub>),  $A + B$  (F<sub>6</sub>),  $\overline{A+B}$  (F<sub>7</sub>),  $\bar{B}$  (F<sub>8</sub>),  $\bar{A}$  (F<sub>12</sub>),  $\overline{A \cdot B}$  (F<sub>13</sub>), Identity (F<sub>15</sub>)

Digital Logic Design - Chapter 2

10

## Sixteen 2-Variable Functions

Boolean Function	Operator Symbol	Name	Comments
F <sub>0</sub> = 0		NULL	binary constant 0
F <sub>1</sub> = $xy$	$x \cdot y$	AND	x and y
F <sub>2</sub> = $xy'$	$x/y$	Inhibition	x, but not y
F <sub>3</sub> = x		Transfer	x
F <sub>4</sub> = $x'y$	$y/x$	Inhibition	y, but not x
F <sub>5</sub> = y		Transfer	y
F <sub>6</sub> = $xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y, but not both
F <sub>7</sub> = $x + y$	$x + y$	OR	x or y
F <sub>8</sub> = $(x + y)'$	$x \downarrow y$	NOR	not-OR
F <sub>9</sub> = $xy + x'y'$	$(x \oplus y)'$	Equivalence (XNOR)	x equals y
F <sub>10</sub> = $y'$	$y'$	Complement	not y
F <sub>11</sub> = $x + y'$	$x \supset y$	Implication	if y, then x
F <sub>12</sub> = $x'$	$x'$	Complement	not x
F <sub>13</sub> = $x' + y$	$x \supset y$	Implication	if x, then y
F <sub>14</sub> = $(xy)'$	$x \uparrow y$	NAND	not-AND
F <sub>15</sub> = 1		Identity	Binary constant 1

Digital Logic Design - Chapter 2

11

## Precedence of Operators

- Precedence of Operator Evaluation (Similar to decimal arithmetic)

- () : Parentheses
- NOT
- AND
- OR

$$F = A \cdot (B + \overline{C \cdot D}) + \bar{A} \cdot \overline{B + E}$$

Diagram illustrating operator precedence with numbered steps (1-5) for evaluation:

1. Evaluate  $C \cdot D$  (innermost parentheses)
2. Evaluate  $\overline{C \cdot D}$  (NOT)
3. Evaluate  $B + \overline{C \cdot D}$  (OR)
4. Evaluate  $A \cdot (B + \overline{C \cdot D})$  (AND)
5. Evaluate  $\bar{A} \cdot \overline{B + E}$  (AND, with  $\bar{A}$  and  $\overline{B + E}$  evaluated separately)

Digital Logic Design - Chapter 2

12

## Function Evaluation

$$F = A \cdot \overline{(B + \overline{C} \cdot D)} + \overline{A} \cdot \overline{\overline{B}} + E$$

ABCDE=00000

$$\begin{aligned} F &= 0 \cdot (\overline{0 + \overline{0} \cdot 0}) + \overline{0} \cdot \overline{\overline{0}} + 0 = 0 \cdot (\overline{0 + 1 \cdot 0}) + \overline{0} \cdot 1 + 0 \\ &= 0 \cdot (\overline{0 + 0}) + 1 \cdot 1 = 0 \cdot 1 + 1 \cdot 0 = 0 \end{aligned}$$



ABCDE=10000

$$\begin{aligned} F &= 1 \cdot (\overline{0 + \overline{0} \cdot 0}) + \overline{1} \cdot \overline{\overline{0}} + 0 = 1 \cdot (\overline{0 + 1 \cdot 0}) + 0 \cdot 1 + 0 \\ &= 1 \cdot (\overline{0 + 0}) + 0 \cdot 1 = 1 \cdot 1 + 0 \cdot 0 = 1 \end{aligned}$$

Digital Logic Design - Chapter 2

13
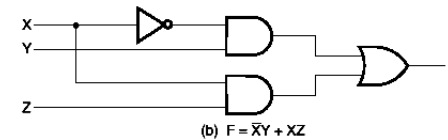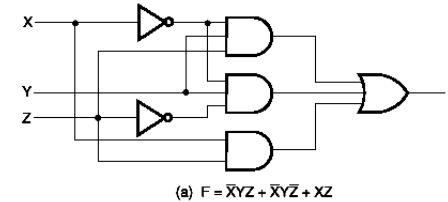
## Implementation of Boolean Function with Gates



Digital Logic Design - Chapter 2

14

## Boolean Variables

- A multi-dimensional space spanned by a set of  $n$  Boolean variables is denoted by  $\mathcal{B}^n$
- A literal is an instance (e.g.  $A$ ) of a variable or its complement ( $\overline{A}$ )

Digital Logic Design - Chapter 2

15

## Basic Identities of Boolean Algebra

$X + 0 = X$	(Identity)
$X + 1 = 1$	
$X + X = X$	(Idempotent Law)
$X + \overline{X} = 1$	(Complement)
$\overline{\overline{X}} = X$	(Involution Law)
$X + Y = Y + X$	(Commutative)
$X + (Y + Z) = (X + Y) + Z$	(Associative)
$X(Y + Z) = XY + XZ$	(Distributive)
$\overline{X + Y} = \overline{X} \overline{Y}$	(DeMorgan's Law)
$X + XY = X$	(Absorption Law)
$X + \overline{X}Y = X + Y$	(Simplification)
$XY + \overline{X}Z + YZ = XY + \overline{X}Z$	(Consensus Theorem)

Digital Logic Design - Chapter 2

16

### Derivation of Simplification

$$\begin{aligned}
 &X + \bar{X}Y \\
 &= X \cdot (1 + Y) + \bar{X}Y \\
 &= X + XY + \bar{X}Y \\
 &= X + (X + \bar{X})Y \\
 &= X + Y \\
 &\therefore X + \bar{X}Y = X + Y
 \end{aligned}$$

Digital Logic Design - Chapter 2

17

### Derivation of Consensus Theorem

$$\begin{aligned}
 &XY + \bar{X}Z + YZ \\
 &= XY + \bar{X}Z + YZ \cdot (X + \bar{X}) \\
 &= XY + \bar{X}Z + XYZ + \bar{X}YZ \\
 &= XY(1 + Z) + \bar{X}Z(1 + Y) \\
 &= XY + \bar{X}Z \\
 &\therefore XY + \bar{X}Z + YZ = XY + \bar{X}Z
 \end{aligned}$$

Digital Logic Design - Chapter 2

18

### Duality Principle

- A Boolean equation remains valid if we take the dual of the expressions on both sides of the equals sign
- Dual of expressions
  - Interchange 1's and 0's
  - Interchange AND ( $\cdot$ ) and OR ( $+$ )

Digital Logic Design - Chapter 2

19

### Duality Principle

$X + 0 = X$	$X \cdot 1 = X$
$X + 1 = 1$	$X \cdot 0 = 0$
$X + X = X$	$X \cdot X = X$
$X + \bar{X} = 1$	$X \cdot \bar{X} = 0$
$X + Y = Y + X$	$X \cdot Y = Y \cdot X$
$X(Y + Z) = XY + XZ$	$X + Y \cdot Z = (X + Y) \cdot (X + Z)$
$\overline{X + Y} = \bar{X} \cdot \bar{Y}$	$\overline{X \cdot Y} = \bar{X} + \bar{Y}$
$X + X \cdot Y = X$	$X \cdot (X + Y) = X$
$X + \bar{X} \cdot Y = X + Y$	$X \cdot (\bar{X} + Y) = X \cdot Y$
$XY + \bar{X}Z + YZ = XY + \bar{X}Z$	$(X + Y)(\bar{X} + Z)(Y + Z) = (X + Y)(\bar{X} + Z)$

Digital Logic Design - Chapter 2

20

## DeMorgan's Law

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



Digital Logic Design - Chapter 2

21


## Generalized De Morgan's Theorem

- NOT all variables
  - Change  $\cdot$  to  $+$  and  $+$  to  $\cdot$
  - NOT the result
- 
- $F = X \cdot Y + X \cdot Z + Y \cdot Z$
  - $F = !((!X + !Y) \cdot (!X + !Z) \cdot (!Y + !Z))$
  - $F = !(X \cdot Y) \cdot (X \cdot Z) \cdot (Y \cdot Z)$

Digital Logic Design - Chapter 2

22

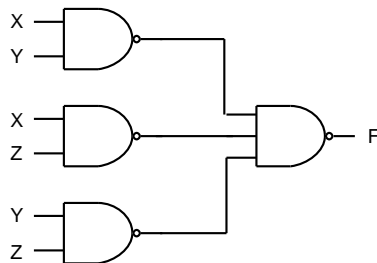
$$F = !((X \& Y) \& (X \& Z) \& (Y \& Z))$$



Digital Logic Design - Chapter 2

23

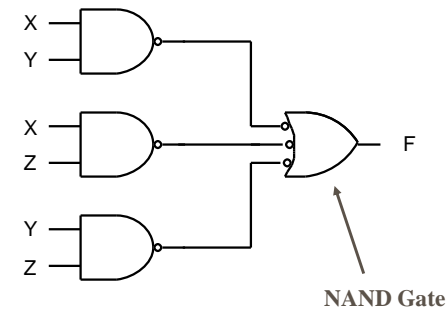
$$F = !((X \& Y) \& (X \& Z) \& (Y \& Z))$$



Digital Logic Design - Chapter 2

24

$$F = X \& Y \mid X \& Z \mid Y \& Z$$

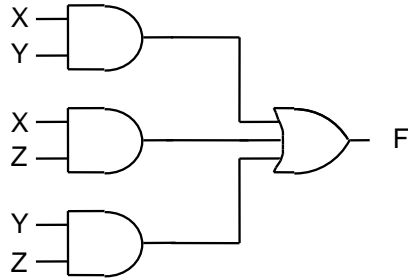

Digital Logic Design - Chapter 2

25

### Sum of Product (SOP) Form

- A product of literals is called a product term (e.g.  $\bar{A} \cdot B \cdot C$  in  $\mathcal{B}^3$ , or  $B \cdot C$  in  $\mathcal{B}^3$ )
- Sum-Of-Product (SOP) Form: OR of product terms is called SOP. e.g.  $\bar{A}B + AC$
- A minterm is a product term in which every literal (or variable) appears in  $\mathcal{B}^n$ 
  - $\bar{A}BC$  is a minterm in  $\mathcal{B}^3$  but not in  $\mathcal{B}^4$ .  $ABCD$  is a minterm in  $\mathcal{B}^4$ .
- A canonical (or standard) SOP function:
  - A sum of minterms, corresponding to the input combination of the truth table, for which the function produces a "1" output.

Digital Logic Design - Chapter 2

26

### Minterms in $\mathcal{B}^3$

			$m_0$	$m_1$	$m_2$	$m_3$	$m_4$	$m_5$	$m_6$	$m_7$
A	B	C	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$	$AB\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}BC$	$A\bar{B}C$	$ABC$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Digital Logic Design - Chapter 2

27

### Canonical (Standard) SOP Function

$$F(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + \bar{A}BC$$

$$= m_0 + m_1 + m_4 + m_5$$

$$F(A,B,C) = \sum m(0, 1, 4, 5) = \text{one-set}(0, 1, 4, 5)$$

$$F(A,B,C,D) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D}$$

$$= m_4 + m_9 + m_{14}$$

$$F(A,B,C,D) = \sum m(4, 9, 14) = \text{one-set}(4, 9, 14)$$

Digital Logic Design - Chapter 2

28

## Product of Sums Design

Maxterms:

A maxterm is a NOT minterm  
maxterm  $M_0$  = NOT minterm  $m_0$

If  $m_0 = (!X \cdot !Y)$

$M_0 = !m_0$

$= !(!X \cdot !Y)$

$= !!X + !!Y$

$= X + Y$

Digital Logic Design - Chapter 2

29

## Product Sum (POS) form (dual of SOP form)

- A sum of literals is called a sum term (e.g.  $\bar{A}+B+C$  in  $\mathcal{B}^3$ , or  $(B+C)$  in  $\mathcal{B}^2$ )
- Product-Of-Sum (POS) Form: AND of sum terms is called POS. e.g.  $(\bar{A}+B)(A+C)$
- A maxterm is a sum term in which every literal (or variable) appears in  $\mathcal{B}^n$ 
  - $(\bar{A}+B+C)$  is a maxterm in  $\mathcal{B}^3$  but not in  $\mathcal{B}^4$ .
  - $A+B+C+D$  is a maxterm in  $\mathcal{B}^4$ .
- A canonical (or standard) POS function:
  - A product (AND) of maxterms, corresponding to the input combination of the truth table, for which the function produces a "0" output.

Digital Logic Design - Chapter 2

30

## Product of Sums Design

X	Y	minterms	maxterms
0	0	$m_0 = !X \cdot !Y$	$M_0 = !m_0 = X + Y$
0	1	$m_1 = !X \cdot Y$	$M_1 = !m_1 = X + !Y$
1	0	$m_2 = X \cdot !Y$	$M_2 = !m_2 = !X + Y$
1	1	$m_3 = X \cdot Y$	$M_3 = !m_3 = !X + !Y$

Digital Logic Design - Chapter 2

31

## Maxterms in $\mathcal{B}^3$

			$M_0$	$M_1$	$M_2$	$M_3$	$M_4$	$M_5$	$M_6$	$M_7$
			$A+B+C$	$A+\bar{B}+C$	$\bar{A}+B+C$	$\bar{A}+\bar{B}+C$	$A+B+\bar{C}$	$A+\bar{B}+\bar{C}$	$\bar{A}+B+\bar{C}$	$\bar{A}+\bar{B}+\bar{C}$
A	B	C	$A+B+C$	$A+\bar{B}+C$	$\bar{A}+B+C$	$\bar{A}+\bar{B}+C$	$A+B+\bar{C}$	$A+\bar{B}+\bar{C}$	$\bar{A}+B+\bar{C}$	$\bar{A}+\bar{B}+\bar{C}$
0	0	0	0	1	1	1	1	1	1	1
0	0	1	1	0	1	1	1	1	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	1	1	1	1	1	0	1	1
1	1	0	1	1	1	1	1	1	0	1
1	1	1	1	1	1	1	1	1	1	0

Digital Logic Design - Chapter 2

32



### Canonical (Standard) POS Function

$$F(A,B,C) = (\bar{A} + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C)(A + \bar{B} + \bar{C})(A + \bar{B} + C) \\ = M7 \cdot M6 \cdot M3 \cdot M2$$

$$F(A,B,C) = \prod M(2,3,6,7) = \text{zero for set}(2,3,6,7)$$

$$F(A,B,C,D) = (\bar{A} + B + \bar{C} + \bar{D})(A + \bar{B} + \bar{C} + D)(A + B + C + \bar{D}) \\ = M11 \cdot M6 \cdot M1$$

$$F(A,B,C,D) = \prod M(1,6,11) = \text{zero for set}(1,6,11)$$

Digital Logic Design - Chapter 2

33

### Convert a Boolean to Canonical SOP

- Expand the Boolean equation into a SOP
- Take each product term with a missing literal, say A, and "AND" (•) it with  $(A + \bar{A})$

Digital Logic Design - Chapter 2

34

### Convert a Boolean to Canonical SOP

$$F = \bar{A}\bar{B} + BC \text{ in } \mathcal{B}^3 \\ \Rightarrow F(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + ABC \\ = \sum m(0,1,3,7)$$

	A	B	C	F	
$\bar{A}\bar{B}\bar{C}$	0	0	0	1	← 0
$\bar{A}\bar{B}C$	0	0	1	1	← 1
$\bar{A}BC$	0	1	0	0	
$ABC$	0	1	1	1	← 3
$\bar{A}\bar{B}\bar{C}$	1	0	0	0	
$\bar{A}\bar{B}C$	1	0	1	0	
$\bar{A}BC$	1	1	0	0	
$ABC$	1	1	1	1	← 7

Minterms listed as 1's

Digital Logic Design - Chapter 2

35

### Convert a Boolean to Canonical SOP

$$F = \bar{A}\bar{B} + BC \text{ in } \mathcal{B}^4 \\ \Rightarrow F(A,B,C,D) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD \\ + \bar{A}BC\bar{D} + \bar{A}BCD + ABC\bar{D} + ABCD \\ = \sum m(0,1,2,3,6,7,14,15)$$

$$F = AB + \bar{B}(\bar{A} + \bar{C}) \text{ in } \mathcal{B}^3 \\ \Rightarrow F(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + ABC \\ = \sum m(0,1,4,6,7)$$

Digital Logic Design - Chapter 2

36

### Convert a Boolean to Canonical POS

- Expand Boolean eqn into a POS
  - Use distributive property
- Take each sum term with a missing literal, say A, and OR it with  $A \cdot \bar{A}$

Digital Logic Design - Chapter 2

37

### Convert a Boolean to Canonical POS

$$F = \bar{A}\bar{B} + BC \text{ in } B^3$$

Use  $X + YZ = (X + Y)(X + Z)$  (Distributive)

$$F = \bar{A}\bar{B} + BC$$

$$F = (\bar{A}\bar{B} + B)(\bar{A}\bar{B} + C)$$

$$F = (\bar{A} + B)(\bar{B} + B)(\bar{A} + C)(\bar{B} + C)$$

$$F = (\bar{A} + B + C\bar{C})(\bar{A} + B\bar{B} + C)(A\bar{A} + \bar{B} + C)$$

$$F = (\bar{A} + B + C)(\bar{A} + B + \bar{C})(\bar{A} + B + C)(\bar{A} + \bar{B} + C)(A + \bar{B} + C)(\bar{A} + \bar{B} + C)$$

$$F = (\bar{A} + B + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)(A + \bar{B} + C)$$

$$= \prod M(2, 4, 5, 6)$$

Digital Logic Design - Chapter 2

38

### Convert a Boolean to Canonical POS

$$F = \bar{A}\bar{B} + BC \text{ in } B^3$$

$$F = \bar{A}\bar{B} + BC$$

$$F = (A + \bar{B} + C)(\bar{A} + B + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

$$= \prod M(2, 4, 5, 6)$$

	A	B	C	F
$\bar{A}\bar{B}C$	0	0	0	1
$\bar{A}BC$	0	0	1	1
$A\bar{B}\bar{C}$	0	1	0	0
$ABC$	0	1	1	1
$\bar{A}BC$	1	0	0	0
$ABC$	1	0	1	0
$A\bar{B}C$	1	1	0	0
$ABC$	1	1	1	1

Maxterms listed  
as 0's

Digital Logic Design - Chapter 2

39

### Convert a Boolean to Canonical SOP

$$F = \bar{A}\bar{B} + BC \text{ in } B^3$$

$$\Rightarrow F(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + ABC$$

$$= \sum m(0, 1, 3, 7)$$

	A	B	C	F
$\bar{A}\bar{B}\bar{C}$	0	0	0	1
$\bar{A}\bar{B}C$	0	0	1	1
$\bar{A}BC$	0	1	0	0
$\bar{A}BC$	0	1	1	1
$ABC$	1	0	0	0
$ABC$	1	0	1	0
$ABC$	1	1	0	0
$ABC$	1	1	1	1

Minterms listed  
as 1's

Digital Logic Design - Chapter 2

40

### Convert a Boolean to Canonical POS

$$F = AB + \bar{B}(\bar{A} + \bar{C}) \text{ in } \mathcal{B}^3$$

Use  $X + YZ = (X + Y)(X + Z)$  (Distributive)

$$F = AB + \bar{B}(\bar{A} + \bar{C})$$

$$F = (AB + \bar{B})(AB + \bar{A} + \bar{C})$$

$$F = (A + \bar{B})(B + \bar{B})(A + \bar{A} + \bar{C})(B + \bar{A} + \bar{C})$$

$$F = (A + \bar{B})(\bar{A} + B + \bar{C})$$

$$F = (A + \bar{B} + C\bar{C})(\bar{A} + B + \bar{C})$$

$$F = (A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})$$

$$= \prod M(2, 3, 5)$$

Digital Logic Design - Chapter 2

41

### Convert a Boolean to Canonical SOP

$$F = AB + \bar{B}(\bar{A} + \bar{C}) \text{ in } \mathcal{B}^3$$

$$\Rightarrow F(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

$$= \sum m(0, 1, 4, 6, 7)$$

Digital Logic Design - Chapter 2

42

### Interchange Canonical SOP and POS

#### ■ For the same Boolean equation

- Canonical SOP form is complementary to its canonical POS form

- Use missing terms to interchange  $\Sigma$  and  $\Pi$

#### ■ Examples

- $F(A, B, C) = \Sigma m(0, 1, 4, 6, 7)$

Can be re-expressed by

- $F(A, B, C) = \Pi M(2, 3, 5)$


Where 2, 3, 5 are the missing minterms in the canonical SOP form

Digital Logic Design - Chapter 2

43
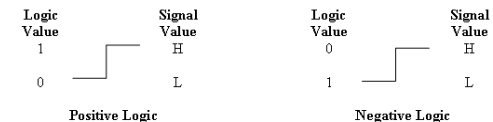
### Positive and Negative Logic

- Binary signals in a circuit can have one of two values.
  - One signal represents logic-1 and the other logic-0.
- A circuit input or output will hold either a high or low signal.
  - Choosing the high level, H, to represent logic-1 is called a positive logic system.
  - Choosing the low level, L, to represent logic-1 is called a negative logic system



Digital Logic Design - Chapter 2

44

## 2-8 Integrated Circuits

- An **integrated circuit (IC)** is a silicon semiconductor crystal, called a chip, containing the electronic components for constructing digital gates.
  - Gates are interconnected within the chip to form the required circuit
  - The IC is housed inside a ceramic or plastic container with connections welded to external pins
  - There can be 14 to several thousand pins on a logic chip
  - Each IC has a numeric designation printed on the surface for identification. The number can be looked up in catalogs (paper and electronic) that contain descriptions and information about the IC

Digital Logic Design - Chapter 2

45

## Levels of Integration

- ICs are categorized by the number of gates that they contain in them:
  - **Small-scale integration (SSI)** devices contain several (usually less than 10) independent gates in a single package.
  - **Medium-scale integration (MSI)** devices include 10 to 1000 gates in a single package, used to perform elementary digital operations.
  - **Large-scale integration (LSI)** devices contain thousands of gates in a single package, used in processors, memory chips, and programmable logic devices.
  - **Very Large-scale integration (VLSI)** devices contain hundreds of thousands of gates in a single package, used in large memory arrays and complex microcomputer chips.

Digital Logic Design - Chapter 2

46

## Logic Families

- ICs are also classified by the specific circuit technology (digital logic family) that they belong to:
  - **Transistor-transistor logic (TTL)** is a standard.
  - **Emitter-coupled logic (ECL)** is used in high-speed operation.
  - **Metal-oxide semiconductor (MOS)** is used for high component density.
  - **Complementary metal-oxide semiconductor (CMOS)** is used in low power consumption.

Digital Logic Design - Chapter 2

47

## Logic Family Characteristics

- Digital logic families are usually compared by the following characteristics:
  - **Fan-out** specifies the amount of current that an output needs to drive many input pins on other gates.
  - **Fan-in** is the number of inputs available in a gate.
  - **Power dissipation** is the power consumed by the gate.
  - **Propagation delay** is the average delay time for the signal to propagate from input to output.
  - **Noise margin** is the maximum external noise voltage added to an input signal that does not cause an undesirable change in the circuit output.
  - **Real estate** is the amount of space required to implement the IC.
  - **Reliability** is the long-term success factor of the IC.

Digital Logic Design - Chapter 2

48