 



CSE 308: Digital System Design

- (a) State whether the following FSM is a Moore/Mealy FSM. Explain why?
- (b) Convert the FSM to its other form.
- (c) Implement the FSM in (a) in Verilog.



Solution:

 - (a) The given FSM is a Mealy FSM because the output depends on present state as well as input.
- (b) Mealy \rightarrow Moore.



(c)

```
module FSM_mealy (clk, reset, in, out);
    input clk, reset, in;
    output out;
    parameter zero = 0, one = 1;
    reg out;
    reg PRSNT_STATE, NXT_STATE;

    // Implement the state register
    always @ (posedge clk)
        if (reset) PRSNT_STATE <= zero;
        else PRSNT_STATE <= NXT_STATE;

    // Implement the combinational logic
    always @ (in or PRSNT_STATE)
        case (PRSNT_STATE)
            zero: begin
                out = in ? 0 : 0;
                NXT_STATE = in ? one : zero;
            end
            one: begin
                out = in ? 1 : 0;
                NXT_STATE = in ? one : zero;
            end
            default: begin
                out = 0;
                NXT_STATE = zero;
            end
        endcase
endmodule;
```

